

I N D E X

Name Shubham Patkar Sub. COR
Std. MCA Div. _____ Roll No. _____

Study of logic Gates & verify their Truth Table.

* AIM: Verification & interpretation of truth table for AND, OR, NOT, NAND, NOR, XOR & XNOR Gates.

* APPARATUS REQUIRED :

SL NO.	Component	Specification	Quantity
1	AND Gate	IC 7408	1
2	OR Gate	IC 7432	1
3	NOT Gate	IC 7404	1
4	NAND Gate	IC 7400	1
5	NOR Gate	IC 7402	1
6	X-OR Gate	IC 7486	1
7	IC Trainer Kit	-	1
8	Patch card	-	As Per require

Theory : Logic Gates are electronic circuits which perform logical functions on one or more I/O to produce 1 o/p.

There are 7 Logic gates. When all I/O combinations of a logic gate are written in a series and their corresponding o/p written along them, this I/O combination is called Truth Table.



Teacher's Signature :


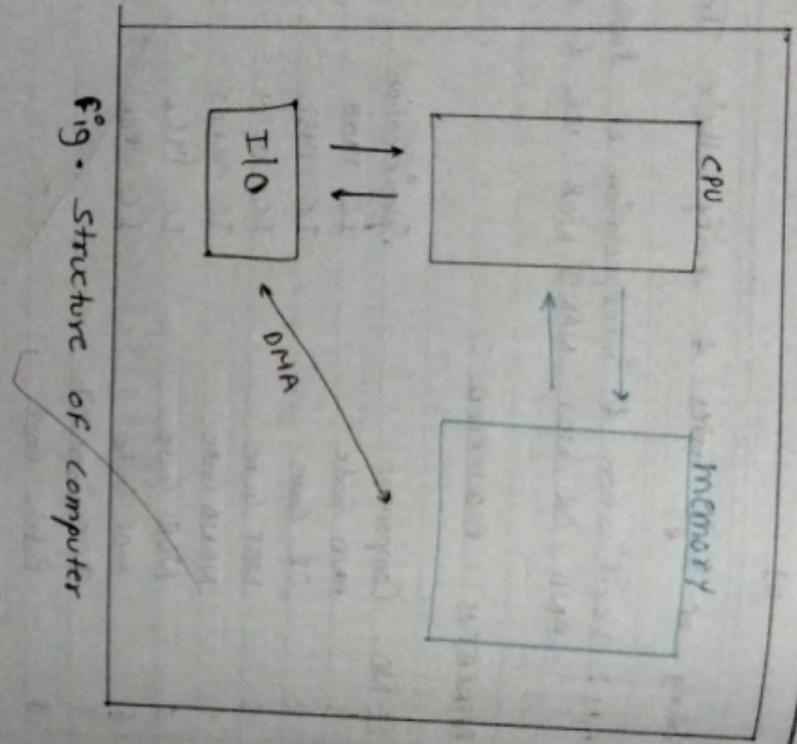


Fig. Structure of computer

- * Program :- A sequence of instruction for the computer is called a program.
- * Logic Gates :- Logic gates are the basic building blocks of any digital system.
- ⇒ It is an electronic circuit having one or more than one I/O & 1 op only.
- ⇒ The relationship b/w the I/O is based on a certain logic.
- ⇒ Gates are blocks of hardware that produce signals of binary 1 or 0 when input logic requirements are satisfied.

Types of Logic Gates

- | | | |
|------------|-------------|------------|
| ① AND Gate | ② OR Gate | ③ NOT Gate |
| ④ NOR Gate | ⑤ NOR Gate | ⑥ NOR Gate |
| ⑦ XOR Gate | ⑧ XNOR Gate | |
- Basic Gates
- Universal Gates
- Exclusive Special Gates

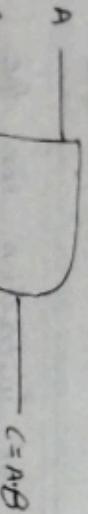

Truth Table

A	B	$C = A \cdot B$
0	0	0
0	1	0
1	0	0
1	1	1



OR GATE

A	B	$C = A + B$
0	0	0
0	1	1
1	0	1
1	1	1

Truth Table

NOT GATE



Truth Table

A	\bar{A}
0	1
1	0



Expt. No. 01

Date 05/01/21
Page No. 03

ii) AND GATE :- In AND gate if it has one false value i.e. 0, then the output is 0 otherwise true i.e. 1.

Boolean expression :- $C = A \cdot B$

→ The algebraic operation symbol of the AND function is the same as the multiplication symbol of ordinary arithmetic.

i) OR GATE :- In OR gate, the output will be 1 if both the inputs are 1 or if only one of both the inputs are 0 otherwise true i.e. 1.


Boolean Expression :- $C = A + B$

→ The algebraic operation symbol of the OR function is the same as the addition operation.

iii) NOT Gate :- It is also known as inverter. It produces the NOT or the complement function. If the input is 1 then output must be 0 & vice-versa.

Boolean Expression :- $C = \bar{A}$

Teacher's Signature:

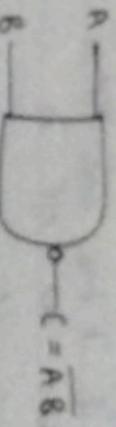

NAND Gate


A	B	$C = \overline{A \cdot B}$
0	0	1
0	1	1
1	0	1
1	1	0



NOR Gate

A	B	$C = \overline{A + B}$
0	0	1
0	1	0
1	0	0
1	1	0


Truth Table

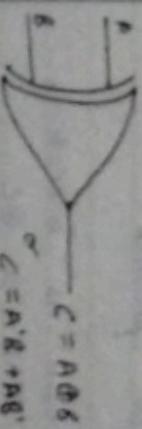

NOT Gate

A	B	$C = A \oplus B$
0	0	0
0	1	1
1	0	1
1	1	0


Truth Table

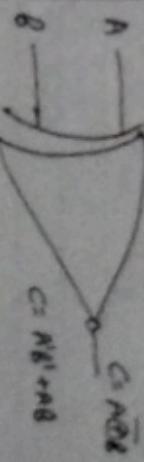

XOR Gate

A	B	$C = A \oplus B$
0	0	0
0	1	1
1	0	1
1	1	0

↓

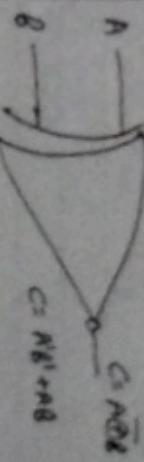Boolean Expression : $C = A \oplus B$ Boolean Expression : $C = A \oplus B$ 

XNOR Gate

A	B	$C = A \oplus B$
0	0	0
0	1	1
1	0	1
1	1	0

XNOR Gate

Boolean Expression : $C = A \oplus B$

XNOR Gate : It is also known as equivalent. It is the inverse of NOR gate.

If both input are same then true L otherwise false O.

Boolean Expression : $C = A \oplus B$

XNOR gate : It is the complement of AND gate.

The XNOR Gate gives an output 0 if both are 1, otherwise 1.


Boolean Expression : $C = A \oplus B$

Truth Table

Expt. No. 01

Page No. 04

Date 05/01/21

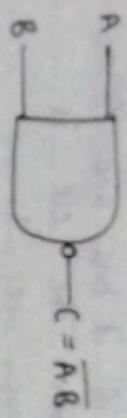

NAND Gate


A	B	$C = \overline{A \cdot B}$
0	0	1
0	1	1
1	0	1
1	1	0



NOR Gate


A	B	$C = \overline{A + B}$
0	0	1
0	1	0
1	0	0
1	1	0

Truth Table

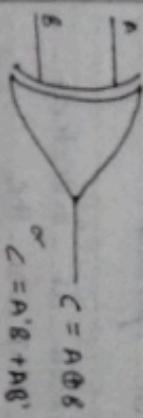

XOR Gate

A	B	$C = A \oplus B$
0	0	0
0	1	1
1	0	1
1	1	0

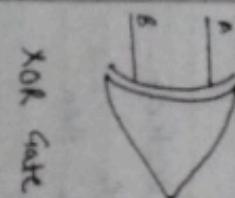

XNOR Gate

A	B	$C = A \oplus \overline{B}$
0	0	1
0	1	0
1	0	1
1	1	0

Boolean Expression

Boolean Expression :- $C = A \oplus B$

Boolean Expression :- $C = A \oplus \overline{B}$

Boolean Expression :- $C = A \oplus B$

v) XNOR gate \rightarrow It is also known as equivalence.

If both inputs are same then true & otherwise false 0.

Procedure:


- * Connect the trainer kit to ac power supply.
- * Connect the ilo of any one logic gate to the logic sources & its o/p to the logic indicator.
- * Apply various ilo combination & observe o/p for each one.
- * Verify the truth table for each ILO combination.
- * Repeat the process for all logic gates.
- * Switch off the dc power supply.

Teacher's Signature : _____



Half - Adder


- Block Diagram

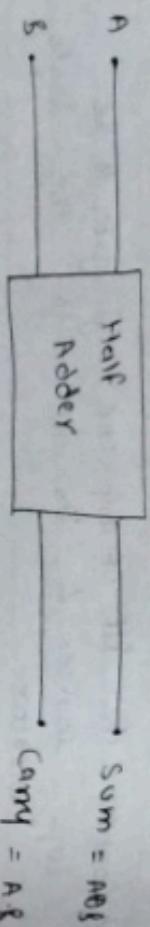

- Truth Table

A	B	Sum	Carry
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

- Logic Diagram

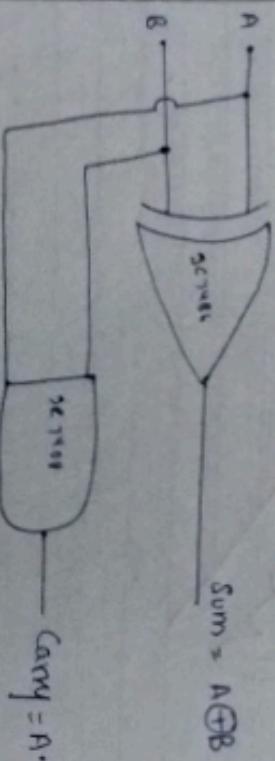

Expt. No. 02 Date 12/10/2012 Page No. 06

- Design & Implementation of full & half adder -

- Aim :- To design & verify logic gates using logic gates.

Sum = A⊕B

Carry = A·B

- Apparatus Required -

IC 7404 (NOT) gate
IC 7408 (AND Gate)
IC 7486 (XOR Gate)
IC 7432 (OR Gate)
Patch cards & trainer kit

- Theory :-

⇒ Half - Adder - It is a combinational circuit that performs the addition of two data bits, A & B.

⇒ Addition will result in two output bits, 1 of which is the sum bit, S and the other is the carry bit, C.

⇒ The Boolean functions describing the half adder are -

$$\text{Sum} = a \oplus b$$

$$\text{Carry} = a \cdot b$$

Teacher's Signature : _____


Expt. No. 52

Page No. 57

A

B

C_{in}

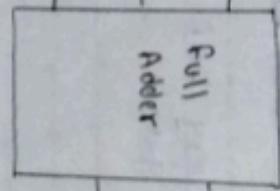

Full
Adder

$$\text{Sum} = A \oplus B \oplus C_{in}$$


Half
Adder

$$\text{Carry} = AB + BC + AC$$

- Truth Table

Input			Output	
A	B	C_{in}	Sum	C_{out}
0	0	0	0	0
0	0	1	1	0
0	1	0	0	0
0	1	1	1	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	1
1	1	1	1	1

- Logic Diagram

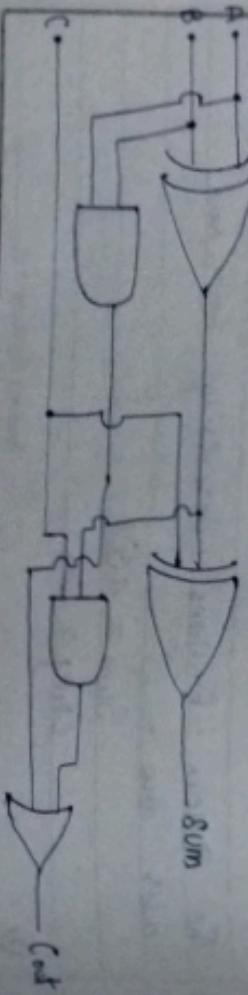

- Logic Diagram

→ Logical expression for Sum

$$\begin{aligned} & A' B' C_{in} + A' B C_{in} + A B' C_{in} + A B C_{in} \\ & C_{in} (A' B' + A B) + C_{in} (A' B + A B') \\ & C_{in} \times OR (A \times OR B) \end{aligned}$$

→ K-map for Sum

	00	01	11	10
0	0	0	1	0
1	0	1	1	1

$$\text{Carry} = A B + B C + A C$$



Teacher's Signature:

Procedure -

- (a) Connections are given as per circuit diagram.
- (b) Logical inputs are given as per circuit diagram.
- (c) Observe the output and verify the truth table.

Q


Output signal



Teacher's Signature :

⑥ Full-Subtractor -


- Block Diagram

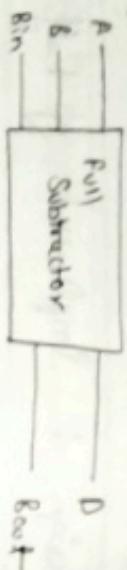

- Truth Table

A	B	B' in	Output	B' out
0	0	0	0	0
0	1	0	1	1
1	0	0	0	1
1	1	0	0	0
0	0	1	1	0
0	1	1	0	0
1	0	1	1	0
1	1	1	0	1

- Logic Diagram

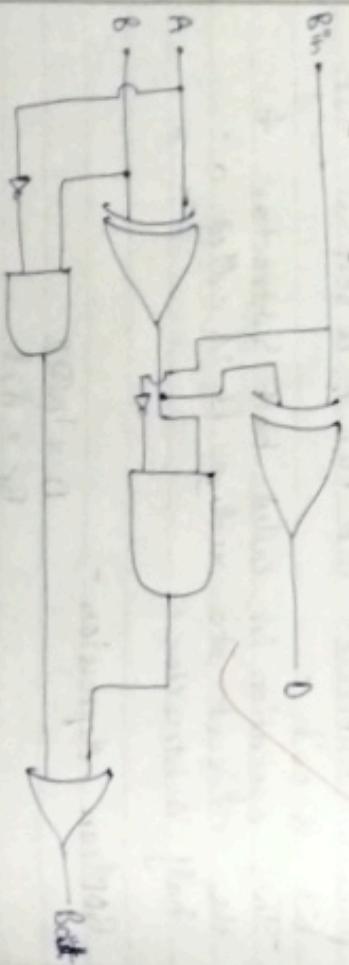

- K-map for B'out -

	0	1
0	0	1
1	1	0

Expt. No. 3
Page No. 10
Date 19/01/21

b) Full Subtractor -

Circuit that performs subtraction of two bits A & B with borrow B' in to produce a difference (D), borrow B' out.

Boolean Expression -

$$\begin{aligned}
 D &= B' B'_{in} + B B'_{in} + A' B'_{in} + A B'_{in} \\
 B'_{in} &= (A' B' + A B) + C'_{in}(A' B + A B') \\
 B'_{in} &= (A \text{ XOR } B)' + B'_{in} (A \text{ XOR } B) \\
 B'_{in} &= (A \text{ XOR } B) \text{ XOR } B'_{in}
 \end{aligned}$$

Procedure -

- Connections are given as per circuit diagram.
- Logical input are given as per circuit diagram.
- Observe the output & verify the truth table.

$$B'_{out} = A B'_{in} + A' B + B'_{in}$$

Teacher's Signature:

Fig: - Logic circuit of 4×1 multiplexer

S_1 S_0 2-bit select 2-bit data input

and and and and

Expt No 63


Date _____

Page No. 12

- Multiplexers are of 4 types -
 - (a) 2×1 multiplexers (2 selection lines)
 - (b) 4×1 (2 " " "
 - (c) 8×1 (3 " " "
 - (d) 16×1 (4 " " "
- One of these 4 inputs will be connected to the output based on the combination of input present at their two selection lines.
- we can implement the Boolean function of 4:1 mux using inverters AND gates & OR gates.

Q3


Teacher's Signature: _____

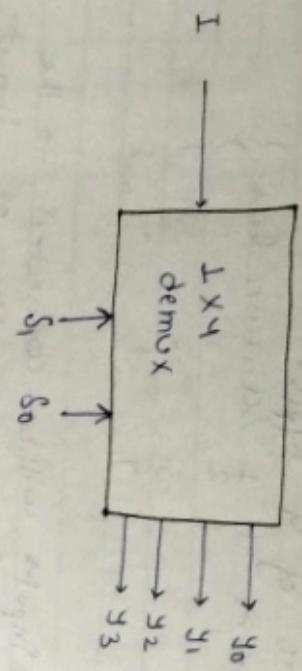

- Truth Table

Selection input	output	↓			
S ₁	S ₀	y ₃	y ₂	y ₁	y ₀
0	0	0	0	0	1
0	1	0	0	1	0
1	0	0	1	0	0
1	1	1	0	0	0

- Circuit diagram

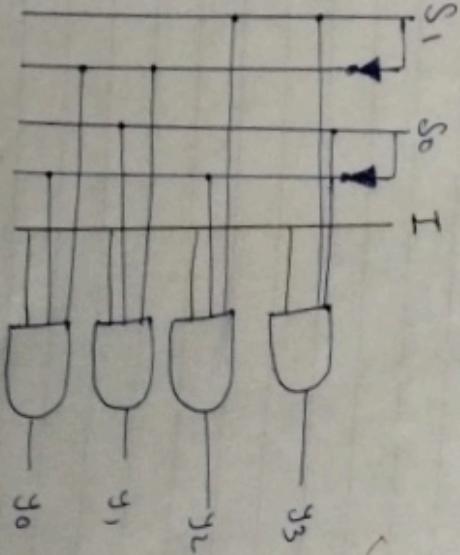

→ Since, there are 'n' selection lines there will be 2^n possible combinations of zeros & ones. So each combination can select only one output.

Demultiplexer is also called as Demux.

1x4 De-Multiplexer - 1x4 demultiplexer has

Input I, 2 selection lines S₁, S₀ & 4 outputs y₃, y₂, y₁, y₀.

* The single input I will be connected to one of the 4 outputs y₃ to y₀ based on the values of selection lines S₁ & S₀. We can implement these boolean functions using inverters & 3 inputs AND gates.

• Procedure -

- 1 Check for the proper working of the Gate.
- 2 Connect the circuit as per circuit diagram
- 3 Verify it with truth table

Result 1 - Study of 4x1 mux & verify truth table.

Result 2 - Study of 1x4 demux & verify TT

Precautions -

- 1 All IC's should checked before starting the experiment.
- 2 All the connection should be tight.
- 3 Always connect the ground first & then connect Vcc.
- 4 Suitable type of wire should be used
- 5 The Kit should be off before change.

Ans ↗



Teacher's Signature : _____